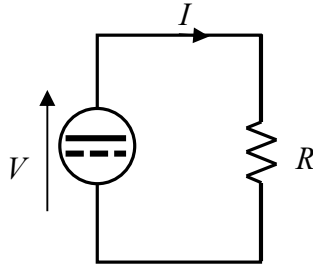


## Resistance and Impedance

### DC circuits



#### Ohm's Law




$$I = V/R \quad - \quad \text{Ohm's law}$$

$$P = IV = V^2/R = I^2 R$$


#### Combining resistances

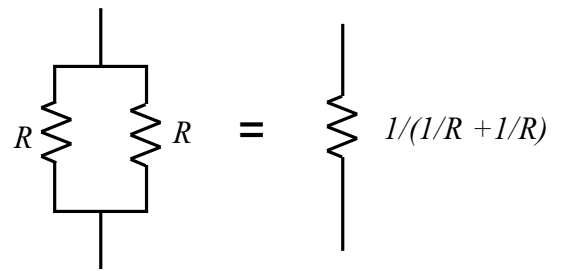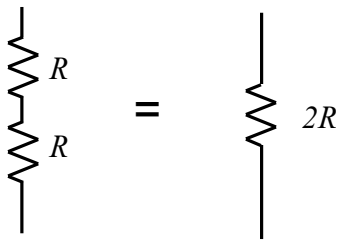

#### Dividers

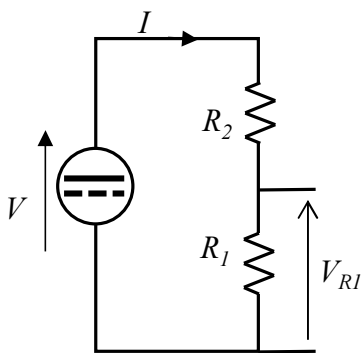


$$V_{R1} = V R_1 / (R_1 + R_2)$$

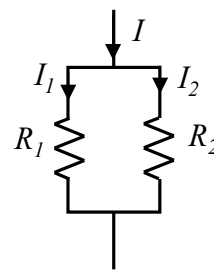


$$I_1 = I R_2 / (R_1 + R_2)$$

Peak power

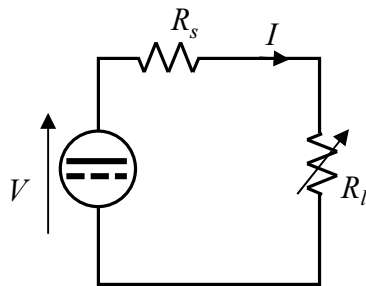

Peak power in  $R_l$  occurs when  $R_l = R_s$

## AC Circuits

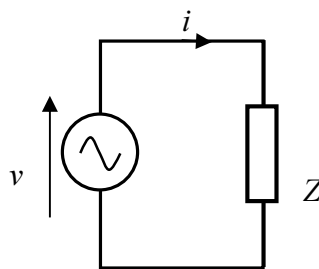

The voltage is given by

$$v = \sqrt{2}V_{rms} \sin(\omega t)$$

The impedance is given by;

$$Z = R + jX$$

Where  $X$  is the reactance and;

$$\text{for Inductance, } L, \quad X = \omega L, \quad \text{for Capacitance } C, \quad X = -\frac{1}{\omega C}$$

In phasor notation we have;

$$\bar{V} = \hat{V} \angle 0 \quad \text{and} \quad \bar{Z} = |Z| \angle \theta$$

$$\text{where } \hat{V} = v_{peak}, \quad |Z| = \sqrt{R^2 + X^2} \quad \text{and} \quad \theta = \tan^{-1} \frac{X}{R}$$

From the phasor form of Ohms law;

$$\bar{I} = \frac{\bar{V}}{\bar{Z}}$$

$$\bar{I} = \frac{\hat{V} \angle 0}{|Z| \angle \theta} = \frac{\hat{V}}{|Z|} \angle -\theta$$

This gives the instantaneous value,  $i$ ;

$$i = \sqrt{2} I_{rms} \sin(\omega t - \theta) \quad \text{where } I_{rms} = \frac{\hat{V}}{\sqrt{2}|Z|} = \frac{V_{rms}}{|Z|}$$


$$P = \overline{VI} = |\bar{I}|^2 \operatorname{Re}(Z)$$

No power is dissipated in an inductor or capacitor since  $\operatorname{Re}(Z) = 0$

### *Combining resistances/Dividers*

Combining resistances and dividing circuits all work for AC in the same way as for DC, just with the substitution of Impedances and complex arithmetic

### *Peak Power*

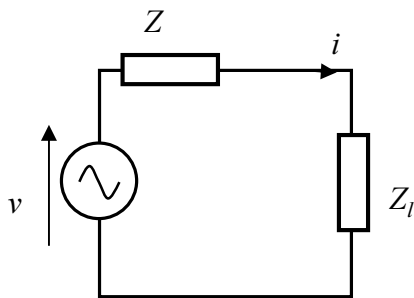

Peak power in  $Z_l$  occurs when  $Z_l$  is complex conjugate of  $Z_s$