


Chapter 4

Pulse Width Modulation, PWM

1

What is PWM Signal ?

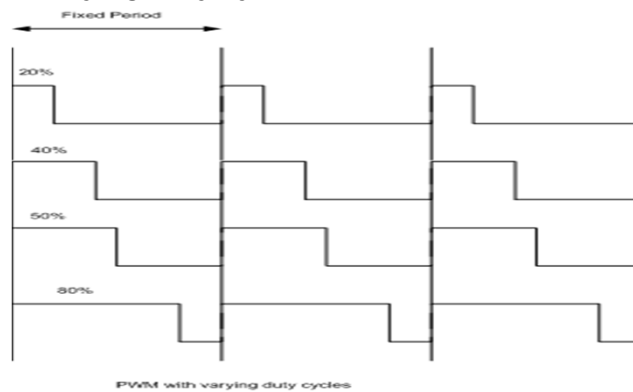- A PWM signal is a digital signal with fixed frequency but varying duty cycle.




2

PWM Applications

- PWM is employed in a wide variety of applications, ranging from measurement and communications to power control and conversion
 - Eg1: Communications:
 - PWM is essentially a means of transmitting information in a series of pulses, where the data being transmitted is encoded on the width of the transmitted pulse
- Eg2: Power Delivery:
 - Reduce the total amount of power delivered to a load
- Examples: DC Motors, Light Dimmers, Anti-Lock, Breaking System.
- Eg3: Voltage Regulation

Applications of PWM (cnt)

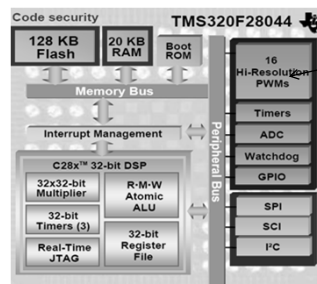- By controlling analogue circuits digitally, system costs and power consumption can be drastically reduced.
- Many microcontrollers and DSPs already include on-chip PWM controllers, making implementation easy.
- e.g.




PWM Generator

Eg: Dimmer using PWM




Simple PWM circuit

PWM 'DAC' Bits

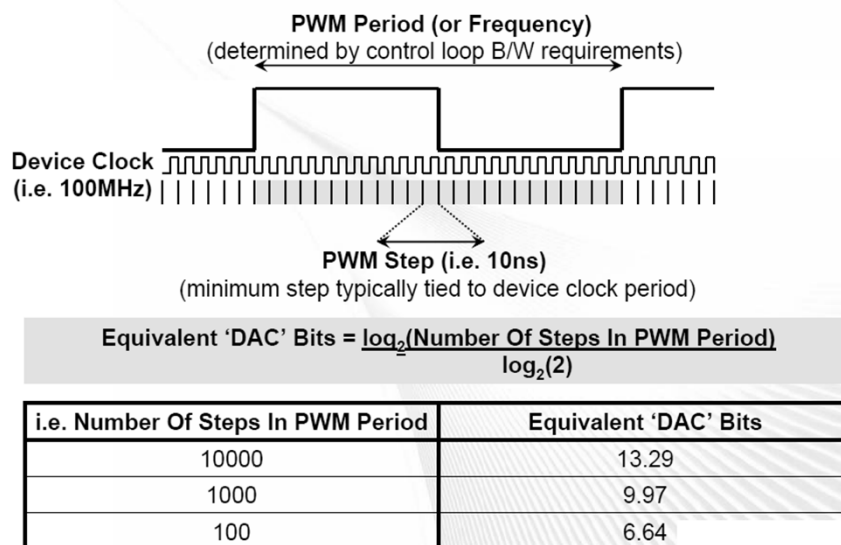


PWM DAC

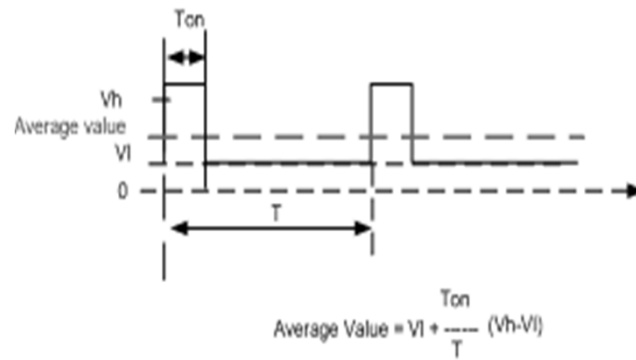- Pulse Width Modulation DAC
Average Value is the Desired Output




PWM DAC

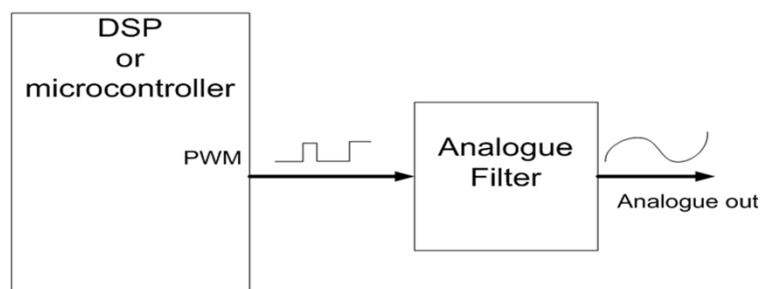

PWM DAC block diagram

PWM DAC Resolution

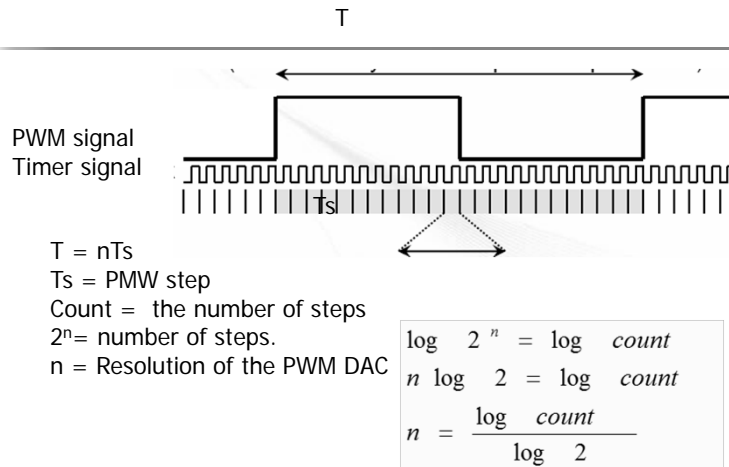

PWM DAC Frequency


- The update rate of the ADC is equivalent to the frequency of the PWM output.
- The frequency of the PWM signal and the desired resolution are required to calculate the frequency of the PWM timer.

$$f_{\text{clock}} = f_{\text{PWM}} \times 2^n$$


f_{clock} = Required PWM timer frequency.

f_{PWM} = PWM signal frequency = DAC rate.

Filtering the PWM signal

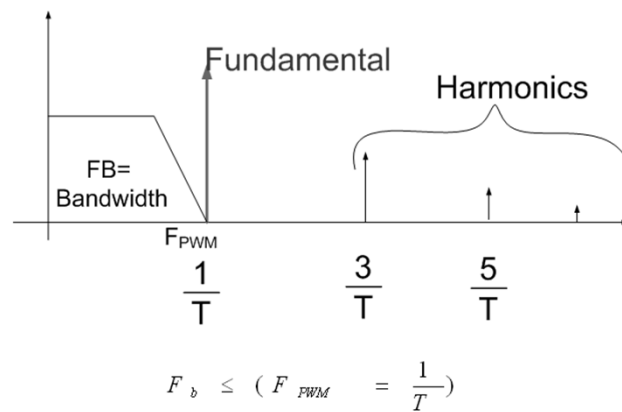

Filtering the PWM signal

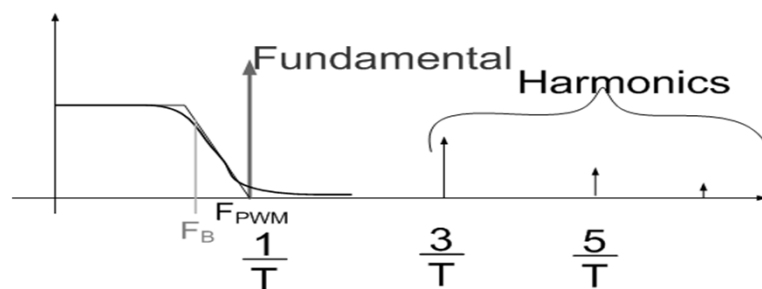

$$F_{PWM} = K F_B \quad \text{with } k \gg 1$$

Eg if $K = 5$ and $F_B = 4 \text{ kHz}$
 Than $F_{PWM} = 5 \times 4 \text{ kHz} = 20 \text{ kHz}$

PWM Filter

Low-pass filters can be built with resistor-capacitor combinations:

The corner frequency is given by $f = 1/(2\pi RC)$

e.g. $R = 160\ \Omega$, $C = 1\ \mu\text{F}$, $f = 1000\ \text{Hz}$.

In practical situation many filters are cascaded to increase the order of the filter and subsequently attenuate the fundamental and harmonics

