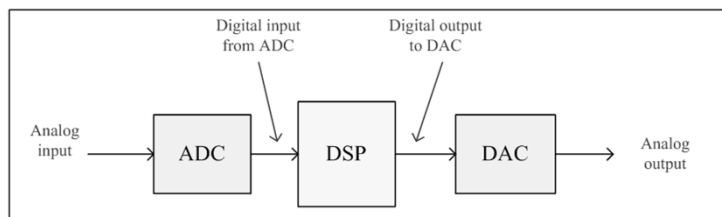


	<p style="text-align: center;"> <b>■ Chapter 6:</b>  <b>■ Analogue-to-Digital Converters</b>  <b>and</b>  <b>Digital-to-Analogue Converters</b> </p>
	<p style="text-align: center;">Analogue to Digital and Digital to Analogue conversions</p>
	1

	<p style="text-align: center;"> <b>Analogue-to-digital converters</b>  <b>and</b>  <b>Digital-to-Analogue converters</b> </p>
	<p> <b>■ Problems:</b>          Analogue signals cannot be interfaced directly to a digital system like a microprocessor or a PC.          Similarly, digital signals cannot be interfaced directly to an analogue system.       </p> <p> <b>■ Solutions:</b>          To solve this problem we need some means to convert and analogue signal to a digital signal and vice versa.          These are achieved by using Analogue to Digital Converters (ADC) and Digital to Analogue Converters (DAC)       </p>
	<p style="text-align: center;">Analogue to Digital and Digital to Analogue conversions</p>
	2


# DSP System



Analogue to Digital and Digital to Analogue conversions

3


# Analogue to Digital Converter

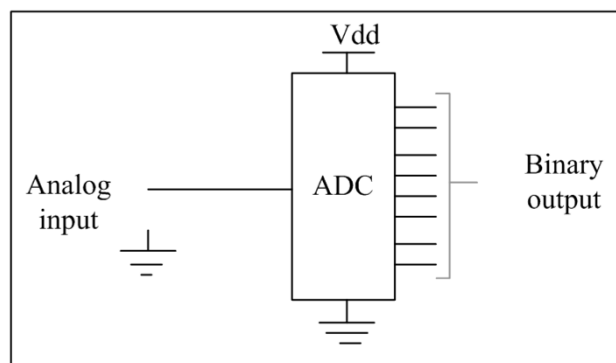

Analogue to Digital and Digital to Analogue conversions

4

## Digital to Analogue Converter

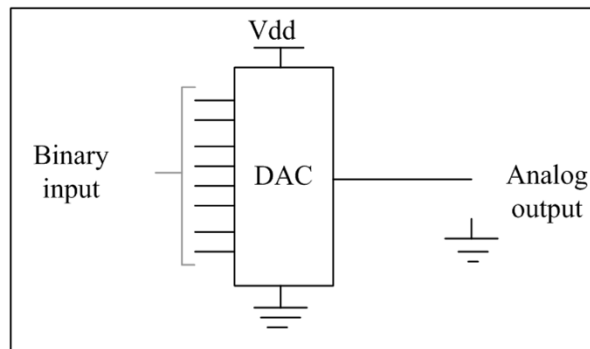

Analogue to Digital and Digital to Analogue conversions

5


## Part 1: Analogue to digital converters

- Flash ADC
- Digital Ramp ADC
- Successive Approximation ADC


Analogue to Digital and Digital to Analogue conversions

6

# Flash ADC

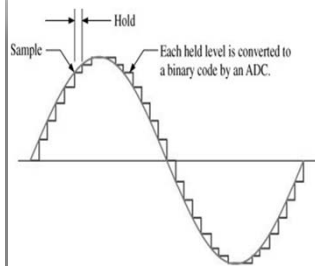


Flash ADC also known as Parallel ADC

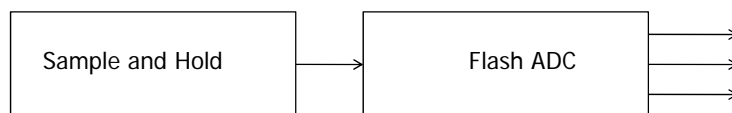

Analogue to Digital and Digital to Analogue conversions

7

# Flash ADC or Parallel ADC

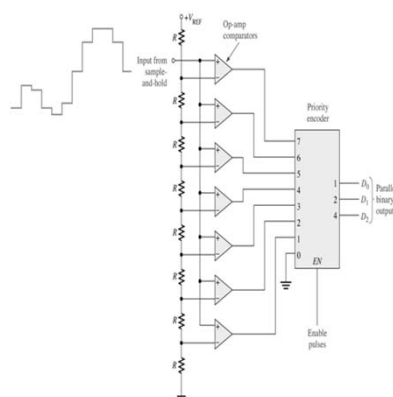

Principle of operation: The input is compared to a set of reference voltages simultaneously

1. Fastest ADC
2. Consume a lot of power.
3. Low resolution

Analogue to Digital and Digital to Analogue conversions

8

# Priority encoder

The true table for an 8 to 3-bit priority encoder.


X = don't care

Inputs								Outputs		
D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	x	0	0	1
0	0	0	0	0	1	x	x	0	1	0
0	0	0	0	1	x	x	x	0	1	1
0	0	0	1	x	x	x	x	1	0	0
0	0	1	x	x	x	x	x	1	0	1
0	1	x	x	x	x	x	x	1	1	0
1	x	x	x	x	x	x	x	1	1	1

Analogue to Digital and Digital to Analogue conversions

9

# Flash ADC or Parallel ADC

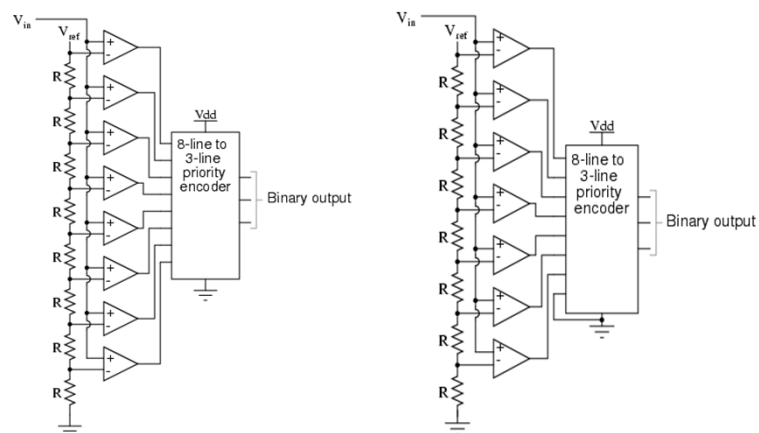

Analogue to Digital and Digital to Analogue conversions

10

# Flash ADC or Parallel ADC

## Advantages

- Very fast

## Disadvantages


1. Needs many comparators.  
(8 comparators for 3-bit ADC)  
(255 comparators for 8-bit ADC)
2. Expensive
3. Large power consumption

Analogue to Digital and Digital to Analogue conversions

11
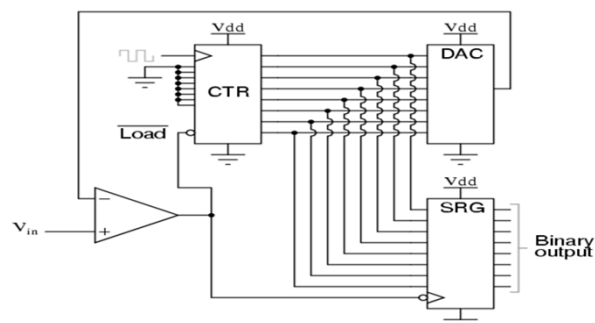
# Digital Ramp ADC

The ADC is built from a DAC as DACs are easier to design



Analogue to Digital and Digital to Analogue conversions


12

## Successive Approximation ADC, SAR ADC

1. Improvement from the RAMP ADC.
2. The main difference is the improvement of the counter which is replaced by a successive approximation Register

### Applications:

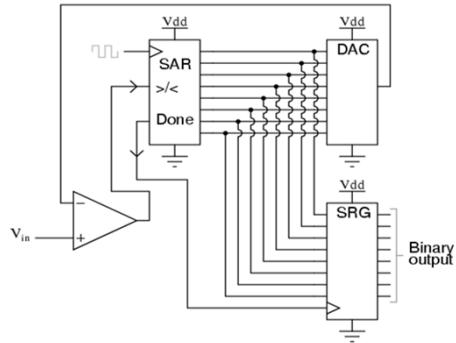
1. Medium-to-high-resolution applications.
2. SAR ADCs most commonly range in resolution from 8- to 16-bits and provide low power consumption as well as a small form factor



Analogue to Digital and Digital to Analogue conversions

13

## Operation of the SAR ADC

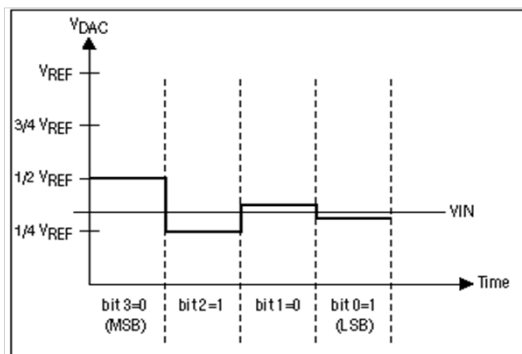

bit 3	bit 2	bit 1	bit 0
0	0	0	0
0	1	0	0
0	1	0	0
0	1	0	1

Note: the successive approximation ADC is much faster than the RAMP ADC, since the counter does not reset to zero for every conversion.

Analogue to Digital and Digital to Analogue conversions

14

## Part 2: Digital to Analogue converters

- R/2nR DAC


- PWM DAC

Analogue to Digital and Digital to Analogue conversions

15

## R/2nR DAC

*Inverting summer circuit*

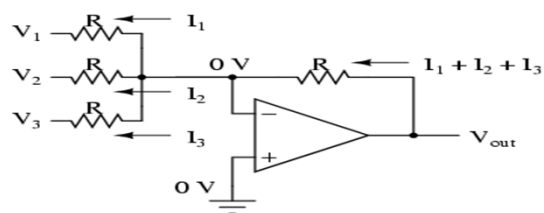


$$V_{out} = -(V_1 + V_2 + V_3)$$

Analogue to Digital and Digital to Analogue conversions

16



## R/2nR DAC

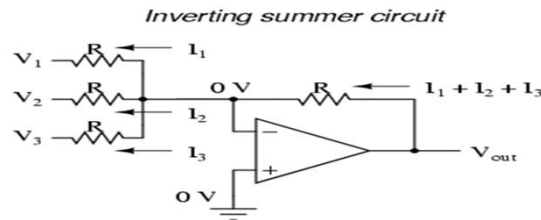

$$V_{out} = -(V_1 + V_2 + V_3)$$

Eg:

If  $D_1 = 1, D_2 = 0, D_3 = 0$  then  $V_{out} = -V$

If  $D_0 = 0, D_2 = 1, D_3 = 0$  then  $V_{out} = -V$

Therefore 100 or 010 or 001 give the same results.

Is this acceptable?


Analogue to Digital and Digital to Analogue conversions

17
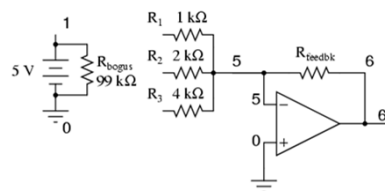
## R/2nR DAC

- The solution is to modify the circuit as shown below:

$$V_{out} = -(D_3 + D_2/2 + D_1/4) V_{ref}$$



MSB	LSB	Vout
0	0	0
0	0	-1/4
0	1	-2/4
0	1	-3/4
1	0	-1
1	0	-5/4
1	1	-6/4
1	1	-7/4

Note: The Resistors R should be very precise

Analogue to Digital and Digital to Analogue conversions

18

## ■ End of Chapter