

	<h2>Boolean Algebra and Combinatorial Logic</h2>
	<p>Part 1: Boolean algebra</p> <p>Part 2: Combinatorial Logic.</p> <p>Learning objectives:</p> <ul style="list-style-type: none"> <li>■ Understanding Boolean algebra.</li> <li>■ Understanding the difference between variable and operator.</li> <li>■ Be able to describe a system by an equation or a truth table.</li> <li>■ Understanding Combinatorial Logic</li> </ul>

1

	<h2>Part 1: Boolean Algebra</h2>
	<ul style="list-style-type: none"> <li>■ Developed by George Boole in the 1850s</li> <li>■ Shannon was the first to use Boolean Algebra to solve problems in electronic circuit design. (1938)</li> </ul>

2

## Variables & Operations

- In Boolean algebra, all variables have the values 1 or 0.  
(sometimes we call the values TRUE or FALSE)
- Basic operators used in Boolean algebra:
  - OR      written as +, e.g. in  $A + B$
  - AND     written as  $\bullet$ , e.g. in  $A \bullet B$
  - NOT     written as an over line or apostrophe, as in  $\overline{A}$  or  $A'$

3

## Operators: OR

- The result of the OR operator is 1 if either of the operands is a 1.
- The only time the result of an OR is 0 is when both operands are 0s.

$a$	$b$	$f(a,b)$
0	0	0
0	1	1
1	0	1
1	1	1

4

## Operators: AND

- The result of an AND is a 1 only when both operands are 1s. Therefore if either operand is a 0, the result is 0.

$a$	$b$	$f(a,b)$
0	0	0
0	1	0
1	0	0
1	1	1

5

## Operators: NOT

- NOT *negates* it's operand.
- If the operand is a 1, the result of the NOT is a 0.
- If the operand is a 0, the result of the NOT is a 1.

$a$	$a'$
0	1
1	0

6

## Equations

Boolean algebra uses equations to express relationships. For example:

$$X = A \cdot (\bar{B} + C)$$

This equation expresses a relationship between the value of ***X*** and the values of ***A***, ***B*** and ***C***.

7

## Quiz

What is the value of each  $X_n$ :

$$X_1 = 1 \cdot (0 + 1)$$

$$X_2 = A + \bar{A}$$

$$X_3 = A \cdot \bar{A}$$

$$X_4 = X_4 + 1$$

8

## Laws of Boolean Algebra

Just like in normal algebra, Boolean Algebra has postulates and identities.

These laws are useful for reducing or simplifying expressions.

9

## Boolean Algebra Laws and Rules

- Boolean algebra uses many of the same laws as those of ordinary algebra.

Commutative law

Distributive law

Associative law

10

## Commutative Laws

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

11

## Distributive Laws

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$$

12

## Associative Laws

$$A (B.C) = (A.B) C$$

$$A + (B + C) = (A + B) + C$$

13

## Other Operators

- Boolean Algebra is defined over the 3 operators AND, OR and NOT.
  - this is a *functionally complete set*.
- However, there are other useful operators:
  - NOR: NOT(OR) is a 0 if either operand is a 1
  - NAND: NOT (AND) is a 0 only if both operands are 1
  - XOR: is a 1 if the operands are different.

14

<b>More Laws!</b>		
$A.B = B.A$	$A + B = B + A$	<b>Commutative law</b>
$A(B + C) = A.B + A.C$	$A + (B + C) = (A + B) + (A + C)$	<b>Distributive law</b>
$A(B.C) = (A.B)C$	$A + (B + C) = (A + B) + C$	<b>Associative Law</b>
$1.A = A$	$0 + A = A$	<b>Identity law</b>
$A.A' = 0$	$A + A' = 1$	<b>Inverse Element</b>
$0.A = 0$	$1 + A = 1$	<b>Null Element</b>
$A.A = A$	$A + A = A$	<b>Idempotent law</b>
$(A.B)' = A' + B'$	$(A + B)' = A'.B'$	<b>De Morgan's Theorem</b>
15		

<b>Boolean Functions</b>	
<ol style="list-style-type: none"> <li>1. Boolean functions are functions that operate on a number of Boolean variables.</li> <li>2. The result of a Boolean function is itself either a 0 or a 1.</li> </ol> <p>Example: <math>f(a,b,c) = (a+b).c</math></p>	
16	



## Alternative Representation

Boolean functions can be represented in two ways:

1. We can define a Boolean function by describing it with algebraic operations (use equation).
2. We can also define a Boolean function by listing the value of the function for all possible inputs (using a truth table)

17

## Truth Table of a Boolean Function

$$f(a,b)=a+b$$

$a$	$b$	$f(a,b)$
0	0	0
0	1	1
1	0	1
1	1	1

18

## Truth Tables

$a$	$b$	OR	AND	NOR	NAND	XOR
0	0	0	0	1	1	0
0	1	1	0	0	1	1
1	0	1	0	0	1	1
1	1	1	1	0	0	0

19

## Truth Table for $(X+Y) \cdot Z'$

X	Y	Z	$(X+Y) \cdot Z'$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

20

## Sum of Products (SOP) and Product of Sums (POS)

		A	B	C		F
0		0	0	0		0
1		0	0	1		1
2		0	1	0		0
3		0	1	1		1
4		1	0	0		1
5		1	0	1		0
6		1	1	0		1
7		1	1	1		1

- :  $F = A'B'C + A'BC + AB'C' + ABC' + ABC$  : Sum of products = SOP
- :  $F = (A+B+C)(A+B'+C)(A'+B+C')$  : Product of Sums = POS

21

## Part 2: Combinatorial Logic


22

## Combinatorial and sequential logic

- **Combinational logic** is a type of logic circuit whose output is only a function of, the present input.
- **Sequential logic** is a type of logic circuit whose output depends not only on the present input but also on the previous inputs.
- Note: sequential logic will NOT be studied in this module

23

## Combinatorial logic

 


n inputs, n is integer greater than one  
m outputs, m is integer greater than one

24


# Combinatorial logic

## ■ Example

 

25

# Sequential logic

 


- Sequential logic has *storage (memory)* while combinational logic does not.

26

# Sequential logic

 - Example:

- Electronics for an Automated teller machine (ATM)**



- a pin number eg: 1342 will be different than 1234


27

# Gates

- Digital logic circuits are electronic circuits that are implementations of some Boolean function(s).
- A circuit is built up of *gates*, each *gate* implements some simple logic function.

28

## A Gate

 


29

## Gates compute something!

- The output depends on the inputs.
- If the input changes, the output might change.
- If the inputs don't change – the output does not change.

30


## An OR gate

 

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

31

## An AND gate

 


A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

32



## A NOT gate

 

A	A'
0	1
1	0

33


## NAND gate



A	B	(A.B)'
0	0	1
0	1	1
1	0	1
1	1	0

34

## NOR gate

 


A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

35

## An XOR gate

A	B	$(A'B) + (AB')$
0	0	0
0	1	1
1	0	1
1	1	0

 


36

## Combinational Circuits

- We can put gates together to produce a circuits
- We can design a circuit that represents any Boolean function!

37

## A Simple Circuit

 

38

## Truth Table for our circuit

$a$	$b$	$\overline{a}$	$\overline{b}$	$\overline{a} \cdot \overline{b}$	$\overline{\overline{a} \cdot \overline{b}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

39

## Alternative Representations


- Any of these can express a Boolean function:

- (1) Boolean Equation
- (2) Circuit (Logic Diagram)
- (3) Truth Table

40

## Integrated Circuits

- You can buy an AND gate *chip*:

 

41

## Function Implementation

- Given a Boolean function expressed as a truth table or Boolean Equation, there are many possible implementations.
- The actual implementation depends on what kind of gates are available.
- In general we want to minimize the number of gates.

42

**Example:**


$$f = A \bullet \bar{B} + \bar{A} \bullet B$$

$A$	$B$	$A \bullet \bar{B}$	$\bar{A} \bullet B$	$f$
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

43

 **One Implementation**

$$f = A \bullet \bar{B} + \bar{A} \bullet B$$




44

## One Implementation


$$f = A \bullet \bar{B} + \bar{A} \bullet B$$

A simplified version

 

45

## Another Implementation

 

$$f = A \bullet \bar{B} + \bar{A} \bullet B = (A + B) \bullet (\bar{A} + \bar{B})$$

46

## Supplement: More example and Applications

47

## Prove $f_1 = f_2$

$$f_1 = A \bullet \bar{B} + \bar{A} \bullet B =$$

$$f_2 = (\bar{A} + \bar{B}) \bullet (A + B)$$

$$A \bullet \bar{B} + \bar{A} \bullet B =$$

$$\overline{(A \bullet \bar{B}) \bullet (\bar{A} \bullet B)} =$$

$$\overline{(\bar{A} + B) \bullet (A + \bar{B})} =$$

$$\overline{((\bar{A} + B) \bullet A) + ((\bar{A} + B) \bullet \bar{B})} =$$

$$\overline{(\bar{A} \bullet A + B \bullet A) + (\bar{A} \bullet \bar{B} + B \bullet \bar{B})} =$$

$$\overline{(B \bullet A) + (\bar{A} \bullet \bar{B})} =$$

$$\overline{(B \bullet A) \bullet (\bar{A} \bullet \bar{B})} =$$

$$\overline{(B + \bar{A}) \bullet (A + B)}$$

$f_1$

DeMorgan's Law

DeMorgan's Laws

Distributive

Distributive

Inverse, Identity

DeMorgan's Law

DeMorgan's Laws


48


 
## Combinational Logic Circuits

- A combinational circuits

- $2^n$  possible combinations of input values



- These circuits implement specific functions such as

- Adders, subtractors, comparators, decoders, encoders, and multiplexers

49


## Decoder

- A circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines
  - At anytime, exactly one output is 1, all others are 0.
- One of the applications of decoder is seven-segment display.

50

## Example: A 3-8 Line decoder

3 inputs are decoded to eight outputs

 

51


## Encoder

- Perform the inverse operation of a Decoder
- A encoder
  - Has  $2^n$  inputs and  $n$  outputs
  - The output lines generate binary code corresponding to the input

52

# Encoder

Inputs				Outputs	
D3	D2	D1	D0	Q1	Q0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x

 

53

# Multiplexer

- A combinational circuit that selects binary information from one of the input lines and directs to a single output line
- The selection of a particular input line is controlled by a set of selection lines.

54


- 2 input mux will need 1 select input to indicate which input to route through
- 4 input mux will need 2 select inputs
- 8 input mux will need 3 select inputs
- N inputs will need  $\log_2(N)$  select inputs

55

## Multiplexer


- 2 input mux will need 1 select input to indicate which input to route through
- 4 input mux will need 2 select inputs
- 8 input mux will need 3 select inputs
- ....
- N inputs will need  $\log_2(N)$  select inputs

- Example:

 

56

## Example: A 4-to-1 line Multiplexer

 


(a) Logic diagram

$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table

57

## Example: A 8-to-1 line Multiplexer

 

58



# Demultiplexer

- Demultiplexer – a circuit that receives information from a single line and directs it to one of the  $2^n$  possible outputs
  - Selection of the output is done by the  $n$  selection lines

A demultiplexer is a decoder with Enable inputs

59

# Demultiplexer

  

60

## Adders

- A Binary adder is a circuit that computes the arithmetic sum of two binary numbers of a given length
- There are several adder circuits
  - Half adder – a combinational circuit that performs addition of 2 bits
  - Full adder – a combinational circuit that performs addition of 3 bits (2 significant bits and a previous carry)
  - Two Half adders can be combined to form a Full adder

61

## The Half Adder

- Adding two 1-bit values results in the following
  - $0+0=0$ ,  $0+1=1$ ,  $1+0=1$  (a sum with 1 bit)
  - and
  - $1+1=10$  (a sum with 2 bits, including a higher significant bit called a carry)
- The Half Adder
  - requires two input variables:  $x$ ,  $y$
  - has two output variables:  $C$  (carry),  $S$  (sum)

$x$	$y$	$C$	$S$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

62


## A Half-Adder Circuit

- The Boolean expressions are:
  - $S = xy' + x'y$
  - $C = xy$
- These can be implemented using
  - AND and OR gates in sum-of-products form
  - XOR and AND gate

63
 
## A Half-Adder Circuit

- The Boolean expressions are:
  - $S = xy' + x'y$
  - $C = xy$



64



## Full-Adder

- A full-adder is to perform the addition of three bits (with previous carry bit, z).
- The Full-Adder has
  - three input bits
    - x, y: two significant bits
    - z: the carry bit from the previous lower significant bit
  - two output bits: C, S

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

65

## Implementing the Adder

- The boolean expressions are:

$$C = x'yz + xy'z + xyz' + xyz$$

$$= z(xy' + x'y) + xy$$

$$S = x'y'z + x'yz' + xy'z' + xyz$$

Implementation using 2 half adders

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

66


## Implementing the Adder

- The boolean expressions are:

$$c = z(xy' + x'y) + xy$$



$$s = x'y'z + x'yz' + xy'z' + xyz$$

Implementation using  
2 half adders

 


## Sequential logic: Example

Example:

  
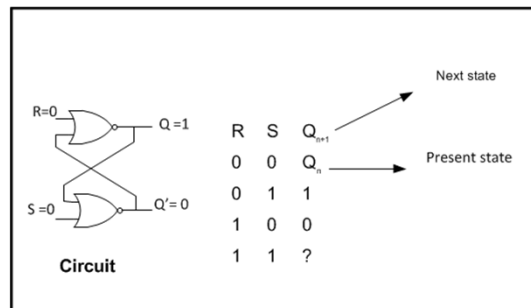
## Sequential logic: SR NOR Latch operation. (flip-flop of latch)

Let's Assume some previous operation has Q as a 1





Simple set-reset latches:

- SR NOR latch
- SR NAND latch
- SR AND-OR latch
- JK latch


69

## D-type flip flop Synchronous latch

  

70

## D-type flip flop Divide-by-2 Counter

 

71